

Roll No.

TEE-301

**B. TECH. (EE) (THIRD SEMESTER)
END SEMESTER EXAMINATION, Dec., 2023**

ELECTRICAL CIRCUIT ANALYSIS

Time : Three Hours

Maximum Marks : 100

Note : (i) All questions are compulsory.

(ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.

(iii) Total marks in each main question are **twenty**.

(iv) Each sub-question carries 10 marks.

1. (a) Explain KVL and Supermesh. Find the currents I_1 and I_2 at the network shown in Fig. 1. (CO1, 2)

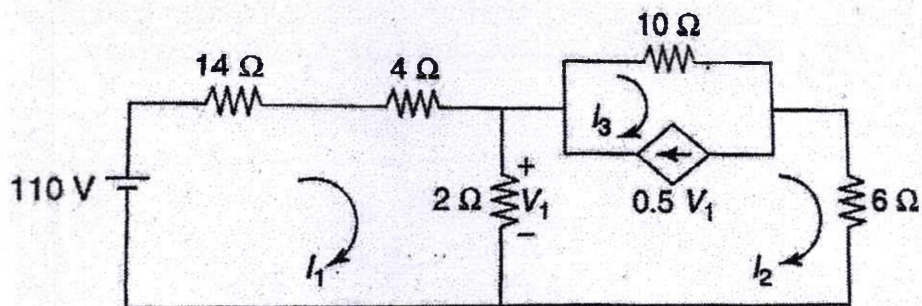


Fig. 1

P. T. O.

(2)

TEE-301

- (b) Determine the current through the 10 ohm resistor in the Fig. 2 using superposition theorem. (CO1, 2)

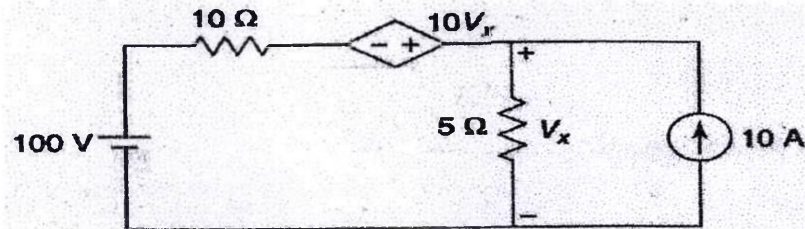


Fig. 2

- (c) For the network shown in Fig. 3, find the value of R_L for maximum power transfer. Also, find the maximum power. (CO1, 2)

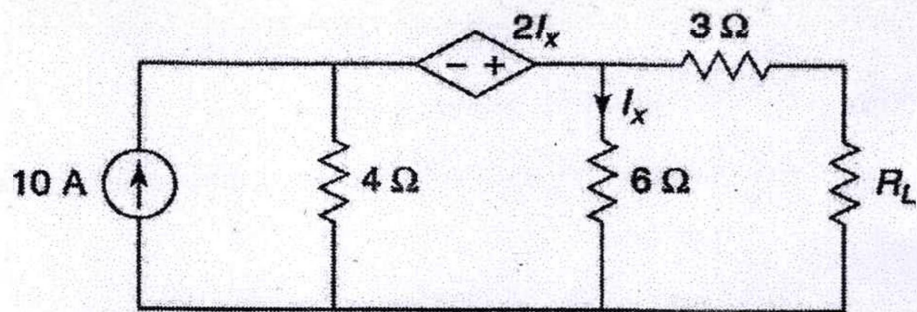


Fig. 3

2. (a) Define the following terms : Planer graph, Connected graph, Rank of a graph, Tree, Co-tree, Directed graph with the help of example. (CO2, 3)
(b) The graph of a network is shown in Fig. 4. Write the (i) incidence matrix, (ii) tieset matrix, and (iii) f - cutset matrix. (CO2, 3)

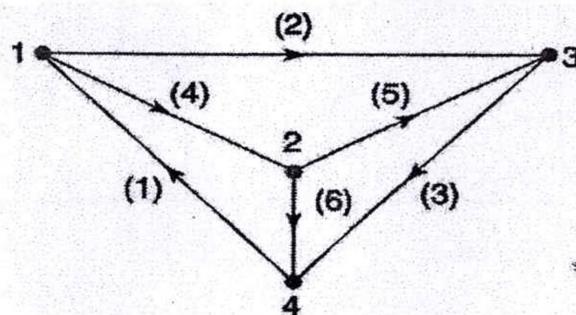


Fig. 4

- (c) A balanced delta-connected load of impedance $(8 - j6)$ ohms per phase is connected to a three-phase, 230 V, 50 Hz supply. Calculate (i) power factor, (ii) line current, and (iii) reactive power. (CO2, 3)
3. (a) The network shown in Fig 5 has acquired steady-state with the switch closed at $t < 0$. At $t = 0$, the switch is opened. Obtain $i(t)$ for $t > 0$ using Laplace transform. (CO4, 5)

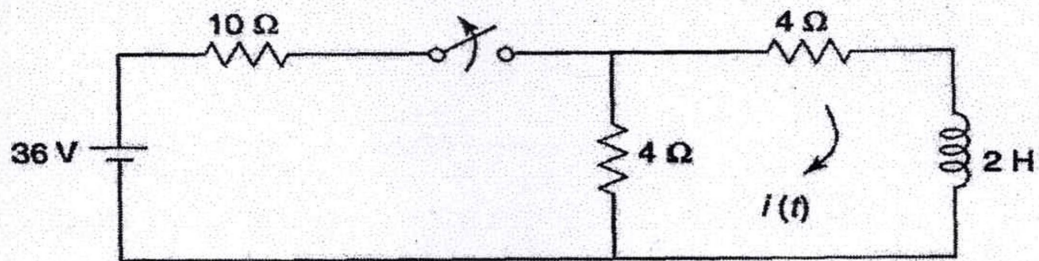


Fig. 5

- (b) Find the current $i(t)$ for the circuit shown in Fig 6. if the voltage source is $v(t) = 5e^{-2t}u(t)$ and $v_c(o-) = 0$. (CO4, 5)

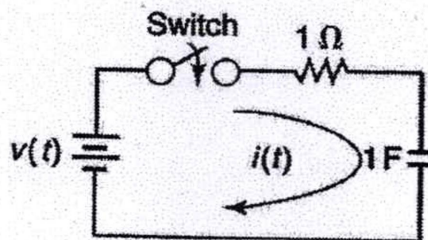


Fig. 6

- (c) Find the inverse Laplace transform of the function : (CO4, 5)

$$F(s) = \frac{12}{(s+2)^2(s+4)}$$

4. (a) Test result for a two-port network are

(i) $I_1 = 0.1 \angle 0^\circ \text{A}$, $V_1 = 5.2 \angle 50^\circ \text{V}$, $V_2 = 4.1 \angle -25^\circ \text{V}$ with port 2 open-

circuited (ii) $I_2 = 0.1 \angle 0^\circ \text{A}$, $V_1 = 3.1 \angle -80^\circ \text{V}$, $V_2 = 4.2 \angle 60^\circ \text{V}$, with

port 1 open-circuited. Find Z-parameters. (CO6)

(b) Find the Z-parameters and Y-parameters of the following network

shown in Fig. 7. (CO6)

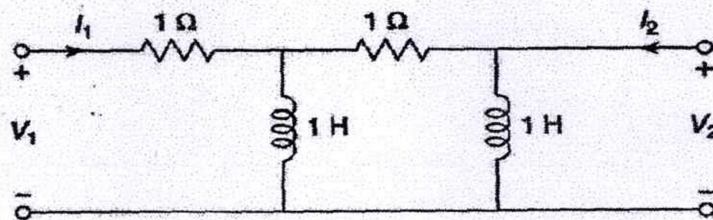


Fig. 7

(c) Determine transmission parameters for the network shown in Fig. 8.

(CO6)

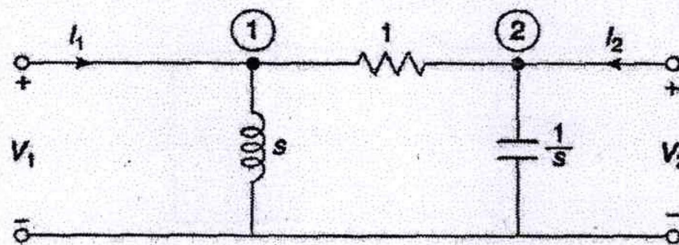


Fig. 8

5. (a) Find the value of R if the average power dissipated in the resistor is

1000 W if the voltage has the following Fourier series :

(CO5)

$$v(t) = 200 \sin \omega t + 100 \sin 3\omega t + 50 \sin 5\omega t$$

(5)

TEE-301

- (b) Find the response voltage in the network shown in Fig. 9. Use Fourier transform method : (CO5)

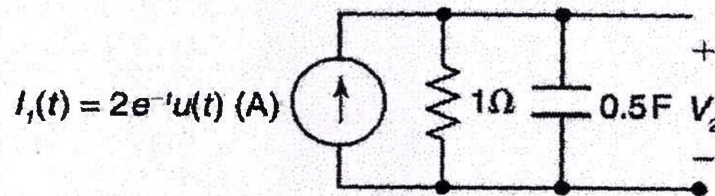


Fig. 9

- (c) A complex wave is given by $i(t) = 10 + 100 \sin \omega t + 40 \sin 5\omega t$. Determine the average value and r.m.s. value of the complex wave.

(CO5)

Roll No.

TEE-302

**B. TECH. (EE) (THIRD SEMESTER)
END SEMESTER EXAMINATION, Dec., 2023**

ELECTRICAL MACHINE-I

Time : Three Hours

Maximum Marks : 100

Note : (i) All questions are compulsory.

(ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.

(iii) Total marks in each main question are **twenty**.

(iv) Each sub-question carries 10 marks.

1. (a) Across the HV side of single phase 200 V/400 V, 50 Hz transformer, an impedance of $32 + j24\Omega$ is connected, with LV side supplied with rated voltage and frequency. Calculate the supply current and the impedance seen by the supply side. (CO3)
- (b) A transformer having core loss and exciting voltamperes at $B_{\max} = 1.5$ T and 60 Hz were found to be $P_{\text{core}} = 16$ W, $(VI)_{\text{rms}} = 20$ VA and induced voltage was $V_{\max} = 242$ when winding had 200 turns, find power factors, core loss current and magnetizing current. (CO3)
- (c) Draw the phasor diagram of transformer at lagging power factor and hence deduce the relation for minimum voltage regulation. (CO3)

P. T. O.

2. (a) A 20 kVA 8000/480 V distribution transformer has the following resistance and reactance : (CO2)

$$X_p = 32 \Omega$$

$$X_s = 45 \Omega$$

$$R_c = 250 \text{ k}\Omega$$

$$R_p = 0.05 \Omega$$

$$R_s = 0.06 \Omega$$

$$X_m = 30 \text{ k}\Omega$$

Find the equivalent circuit of this transformer referred to the high-voltage side. Current in primary as well as secondary.

- (b) Discuss open circuit test and short circuit test of transformer with suitable diagram and obtain the condition for maximum efficiency.

(CO2)

- (c) The equivalent circuit impedances of a 20 kVA, 8000 V/240 V, 60 Hz transformer are to be determined. The open-circuit test and the short-circuit test was performed on the primary side of the transformer, and the following data were taken : (CO2)

Open-circuit test (on primary) $V_{OC} = 8000 \text{ V}$, $I_{OC} = 0.214$, $P_{OC} = 400 \text{ W}$

Open-circuit test (on primary) $V_{SC} = 489 \text{ V}$, $I_{SC} = 2.5 \text{ A}$, $P_{SC} = 240 \text{ W}$

Find the impedances of the approximate equivalent circuit referred to the primary side, and sketch that circuit.

3. (a) List and describe the types of losses that occur in a transformer and hence obtain the condition for maximum efficiency. (CO1)
- (b) A 100-VA 120/12-V transformer is to be connected so as to form a step-up autotransformer (see Figure 1). A primary voltage of 120 V is applied to the transformer. (CO1)
- (i) What is the secondary voltage of the transformer ?
- (b) What is its maximum volt ampere rating in this mode of operation ?

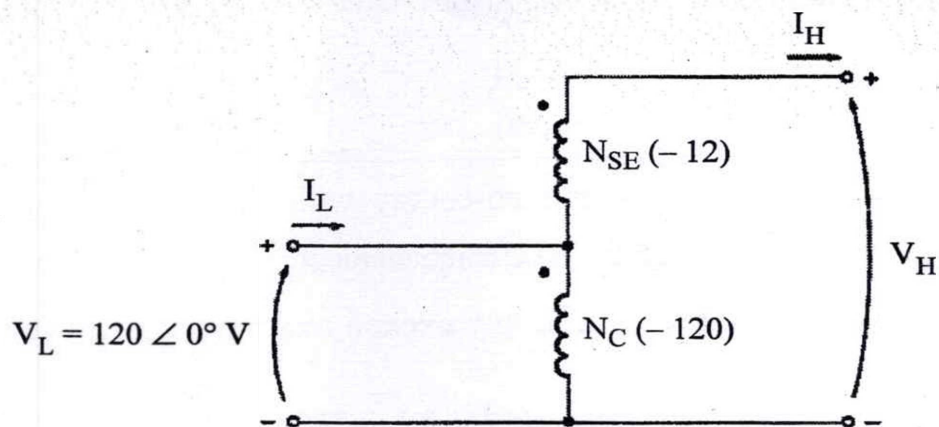


Fig. 1

- (c) A wrought iron bar 30 cm long and 2 cm in diameter is bent into a circular shape as shown in fig. 2 below. It is then wound with 600 turns of wire.

Calculate the current required to produce a flux of 0.5 mWb in the magnetic circuit in the following cases : (CO1)

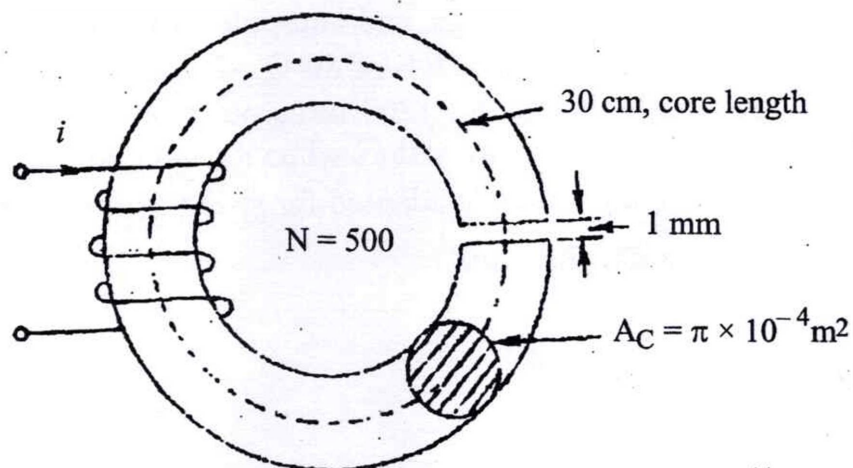


Fig. 2

P. T. O.

- (i) no air-gap;
- (ii) with an air-gap of 1 mm; $\mu_r (\text{iron}) = 4000$ (assumed constant); and
- (iii) with an air-gap of 1 mm; assume following data for the magnetization of iron :

H in At/m	B in T
2500	1.55
3000	1.59
3500	1.6
4000	1.615

4. (a) Discuss energy and co-energy with suitable diagram, why magnetic field is needed for electromechanical energy conversion. (CO1)
- (b) For a system of multiply excited magnetic system various inductances are : (CO1)
 $L_{11} = (4 + \cos 2\theta) \times 10^{-3} \text{ H}$, $L_{12} = 0.15 \cos \theta \text{ H}$, $L_{22} = (20 + 5 \cos 2\theta) \text{ H}$
 find the torque developed if $i_1 = 1 \text{ A}$ and $i_2 = 0.02 \text{ A}$
- (c) Deduce the relation for co-energy and torque for doubly excited magnetic field system. (CO1)
5. (a) What are various types of d.c. machines based on excitation system ? Explain them with suitable diagram. (CO4)
- (b) A 50-hp, 250-V, 1200 r/min d.c. shunt motor with compensating windings has an armature resistance (including the brushes, compensating windings, and interpoles) of 0.06Ω . Its field circuit has a total resistance $R_{\text{adj}} + R_F$ of 50Ω , which produces a no-load speed of 1200 r/min. There are 1200 turns per pole on the shunt field winding. Find the speed of this motors when its input current is 100 A. (CO4)
- (c) What are the methods adopted for speed control of d.c. motor ? Discuss with suitable diagram. (CO4)

Roll No.

TEE-303

**B. TECH. (EE) (THIRD SEMESTER)
END SEMESTER EXAMINATION, Dec., 2023**

ELECTRICAL AND ELECTRONIC MEASURING INSTRUMENTS

Time : Three Hours

Maximum Marks : 100

Note : (i) All questions are compulsory.

(ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.

(iii) Total marks in each main question are **twenty**.

(iv) Each sub-question carries 10 marks.

1. (a) What are the terms measurements and measurement system ? Describe the functional element of measurement system with a block diagram.

(CO1)

(b) Differentiate between electrical, electronic and mechanical instruments with suitable examples.

(CO1)

(c) Explain the following terms :

(CO1)

(i) Accuracy

(ii) Selectivity

(iii) Sensitivity

(iv) Errors

P. T. O.

(2)

2. (a) Discuss briefly about bridges. Draw the Anderson's bridge circuit and derive necessary equations and explain it. (CO2)
- (b) Maxwell bridge is used to measure an inductive impedance the bridge constants at balance are $C_1 = 0.05 \mu\text{F}$, $R_1 = 500 \text{ k}\Omega$, $R_2 = 10.1 \text{ k}\Omega$ and $R_3 = 10 \text{ k}\Omega$. find the series equivalent of the unknown impedance. (CO2)
- (c) How can we increase the range of Ammeter and Voltmeter ? (CO2)
3. (a) Explain different types of instruments transformer. (CO3)
- (b) Explain current transformer and potential transformer with a neat and clean diagram. (CO3)
- (c) Why Kelvin's bridge used ? Explain with diagram. (CO2)
4. (a) Explain digital voltmeter with block diagram. (CO4)
- (b) What is the difference between analog voltmeter and digital voltmeter ? (CO4)
- (c) Write a short note on Flip-flop, Registers and Counters. (CO4)
5. (a) Draw the block diagram of a Cathode ray oscilloscope and explain function of each block in detail of each block in detail. (CO5)
- (b) Explain the major parts of Cathode ray tube with a block diagram. Compare (CO5)
- (c) Explain different types of CRO with block diagram. (CO5)

Roll No.

TEE-304

**B. TECH. (EE) (THIRD SEMESTER)
END SEMESTER EXAMINATION, Dec., 2023**

ELECTROMAGNETIC FIELDS

Time : Three Hours

Maximum Marks : 100

Note : (i) All questions are compulsory.

(ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.

(iii) Total marks in each main question are **twenty**.

(iv) Each sub-question carries 10 marks.

1. (a) Discuss cylindrical co-ordinate system. If A_x, A_y , and A_z are the component of vector A in Cartesian co-ordinate system and A_ρ, A_ϕ , and A_z are component of same vector in cylindrical co-ordinate systems then find the relation between these two components. (CO1)

(b) Determine the divergence of the vector fields : (CO1)

(i) $P = (x^2 yz)a_x + (xz)a_z$


(ii) $Q = (\rho \sin \phi)a_\rho + (\rho^2 z)a_\phi + (z \cos \phi)a_z$

P. T. O.

- (c) Convert a point $P(4, -3, 6)$ and a vector $R = z a_x + y a_z$ into cylindrical coordinate systems. (CO1)
2. (a) Derive the expression of electric field intensity at the perpendicular bisector point of linear charge distribution of charge per unit length ' λ '. Assume the length of linear distribution is ' a ' and distance of the point is $a/2$ from the center of linear charge distribution. (CO2, CO3)
- (b) Discuss Gauss' law. Derive Maxwell equation which is based on Gauss' law. (CO2, CO3)
- (c) Point charges 1 mC and -2 mC are located at $(3, 2, -1)$ and $(-1, -1, 4)$, respectively. Calculate the electric force on a 10 nC charge located at $(0, 3, 1)$ and the electric field intensity at that point. (CO2, CO3)
3. (a) Explain convection and conduction currents. Derive mathematical equations also. Also derive the magnetic vector potential. (CO3, CO4)
- (b) Discuss the following : (CO3, CO4)
- (i) Ohm's law in point
- (ii) Continuity Equation
- (c) If potential (V) at any point is given as (i) $V(x, y, z) = 5x^3y^2z$
(ii) $V(\rho, \phi, z) = z \cos(\phi) / \rho$, then find change per unit volume at $(-3, 1, 2)$ and $(3, 30^\circ, 2)$. (CO3, CO4)
4. (a) State and explain (i) Biot-Savart's Law (ii) Ampere's circuital law. (CO5)

(3)

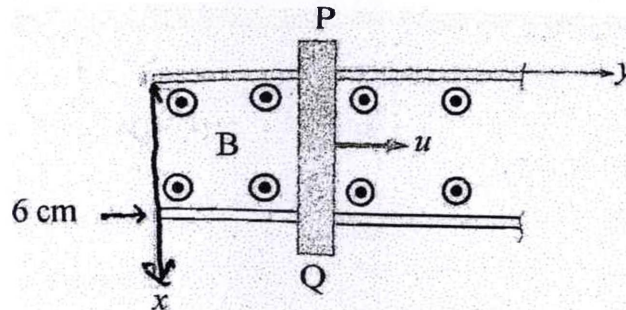- (b) A conductor of length 100 cm moves at right angles to uniform field of strength 1T, with velocity of 50 m/s. Calculate the emf induced in it. Also, calculate the value of induced emf when conductor moves at an angle of 30° to the direction of field. (CO5)
- (c) Discuss Faraday's law of electromagnetic induction. Derive Maxwell equation using Faraday's law of electromagnetic induction. (CO5)
5. (a) Discuss the differential and integral form of Maxwell's equations. (CO6)
- (b) Derive the wave equations for conducting medium. (CO6)
- (c) A conducting bar can slide freely over two conducting rails as shown in figure. Calculate the induced voltage in the bar. (CO6)
- (i) If the bar is stationed at $y = 8$ cm and $B = 4 \cos(10^6 t) a_z$ mWb/m²
- (ii) If the bar slides at a velocity $u = 20 a_y$ m/s and $B = 4 a_z$ mWb/m².



Roll No.

TEE-305

**B. TECH. (EE) (THIRD SEMESTER)
END SEMESTER EXAMINATION, Dec., 2023**

ANALOG ELECTRONICS

Time : Three Hours

Maximum Marks : 100

Note : (i) All questions are compulsory.


(ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.

(iii) Total marks in each main question are **twenty**.

(iv) Each sub-question carries 10 marks.

1. (a) Write a brief note on conductors, insulators and semiconductors.

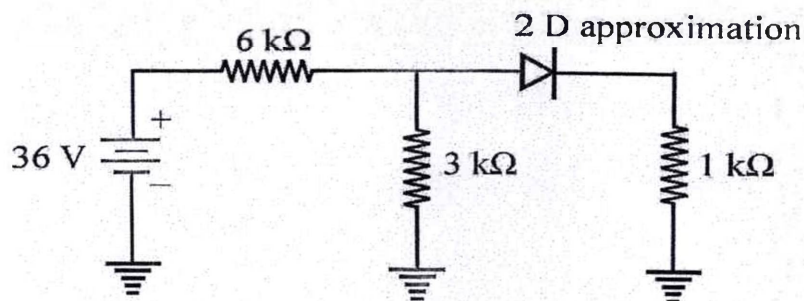(b) Calculate the load voltage, load current and diode power in the following circuit using second approximation :




P. T. O.

(2)

TEE-305

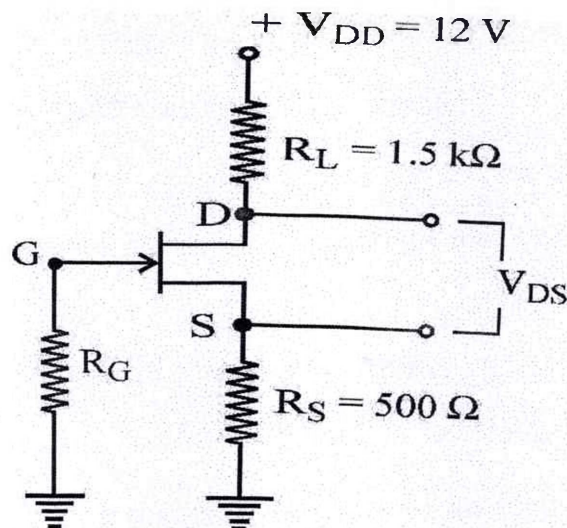
- (c) Draw the circuit diagram of a full-wave bridge rectifier. Write its working with the help of wave shapes.
2. (a) Describe the ways of D. C biasing an FET connected in common source configuration.
- (b) (i) What are the effects of Gate voltage ?
(ii) Explain what purpose R_G serves.
- (c) Find the value of V_{DS} and V_{GS} in the following circuit for $I_D = 4\text{mA}$:



(CO)

3. (a) An NPN transistor is connected in common emitter configuration. (CO)
 $V_{CC} = 30\text{ V}$, $V_{EE} = -30\text{ V}$, $R_L = 10\text{ k}\Omega$, $R_B = 20\text{ k}\Omega$ and $\beta = 100$
Neglect V_{BE} .
Find (i) I_E , (ii) I_B (iii) I_C (iv) V_{CE}
- (b) Answer "True" or "False." If the answer is "false," give the right answer:
- (i) A bipolar transistor consists of three equally doped regions.

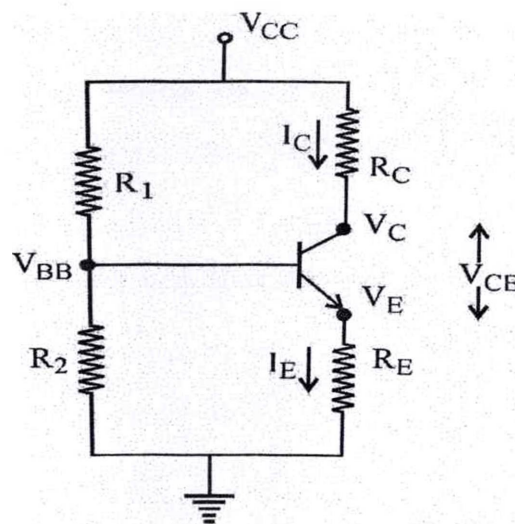
- (ii) In a normally-biased NPN transistor, collector is at higher positive potential than base.
 - (iii) Amongst the three currents of a transistor, I_E is the largest.
 - (iv) Theoretically, the CB configuration of a transistor yields the highest current gain.
 - (v) Temperature- dependent leakage current I_{CO} of a transistor is due to the majority charge carriers.
 - (vi) When in a circuit $I_C = 0$, the transistor is said to be cut-off.
 - (vii) A transistor is said to be saturated when $V_{CE} = 0$.
- (c) In a voltage- divider bias circuit of an NPN transistor as show below :



Write the equation for V_{BB} , V_E , I_E , I_C , V_C and V_{CE} .

4. (a) What is a unity Gain Differential Amplifier ? Draw circuit using an Op-Amp, and write its applications.

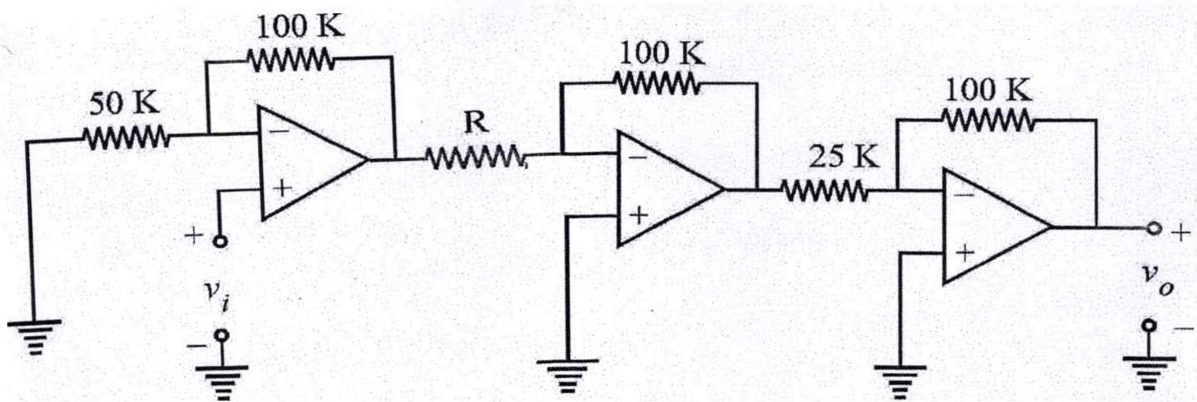- (b) Draw the circuit of a three input summing Amplifier using an Op-Amp in its inverting configuration. Derive expression for the circuit's output V_O .
- (c) In the cascade of ideal OP-Amps, as shown below, of $V_i = 2V$ and $V_o = 30V$, determine the value of R .



5. (a) What are various types of active filters ? Draw their various circuits employing Operational Amplifiers.
- (b) Explain the working of an instrumentation amplifier, employing Operational Amplifiers, with the help of its circuit diagram.
- (c) Draw the circuit diagram of a square wave generator and a triangular wave generator. Explain their working.

Roll No.

VAC-301

**B. TECH. (EE) (THIRD SEMESTER)
END SEMESTER EXAMINATION, Dec., 2023**

BASICS OF MATLAB

Time : Three Hours

Maximum Marks : 100

Note : (i) All questions are compulsory.

(ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.

(iii) Total marks in each main question are **twenty**.

(iv) Each sub-question carries 10 marks.

1. (a) What do you mean by array ? Explain numeric array and character arrays with suitable example. (CO1/CO2)
- (b) Explain the feature of MATLAB. Also discuss its merits and limitations. (CO1/CO2)
- (c) What is simulink ? How do you use it to model and simulate systems ? (CO1/CO2)
2. (a) List some basic plots and graphs of MATLAB. (CO3)
- (b) Discuss the application on the following : (CO3)
 - (i) Bus selector
 - (ii) Bus creator
 - (iii) Scope block used in MATLAB.

P. T. O.

- (c) Write a MATLAB to draw sinusoidal plots of five different magnitude on the same plane. (CO3)
3. (a) Discuss branching and looping function. (CO6)
- (b) Write a MATLAB to generate multiplication table from 1-10. (CO6)
- (c) Write a MATLAB code to determine factorial of number from 1 to 10. (CO6)
4. (a) Using switch and case function, write a MATLAB code to determine area and circumference of the circle. Inputs are radius and case through the command window. (CO5)
- (b) Generate matrix, 'A', as shown below. For the matrix 'A', what will be the output of the following commands : (CO5)
- (i) Sum (diag(A))
- (ii) Sum(diag(fliplr(A)))
- (iii) A (1, 2) + A (3, 3) + A'(2, 2)
- (iv) Sum (A (1 : 3, 2)) + Sum (A (1 : 3, 3))
- $$A = \begin{bmatrix} 20 & 3 & 7 \\ 5 & 5 & 11 \\ 8 & 6 & 7 \end{bmatrix}$$
- (c) Write a program to evaluate the resonant frequency and quality factor of a parallel resonance RLC circuit. The value of R, L, and C are input through the command window. (CO5)

(3)

5. (a) Write the MATLAB code to determine the root of quadratic equation with the following condition : (CO4, CO6)

(i) If ' a ' is not equal to zero

(ii) if ' a ' is equal to zero

The inputs are coefficient of the quadratic equation, i.e., ' a ', ' b ' and ' c '.

- (b) Explain the difference between global and local variables in MATLAB. Also. Explain the difference between a script and a function in MATLAB. (CO4, CO6)

- (c) Write a MATLAB code to determine the sum of numbers from 1 to 100. (CO4, CO6)

