

Roll No.

TEE-301(ECA)

B. TECH. (EE) (THIRD SEMESTER) MID SEMESTER EXAMINATION, Oct., 2022

ELECTRICAL CIRCUIT ANALYSIS


Time : 1½ Hours

Maximum Marks : 50

Note : (i) Answer all the questions by choosing any *one* of the sub-questions.

(ii) Each sub-question carries 10 marks.

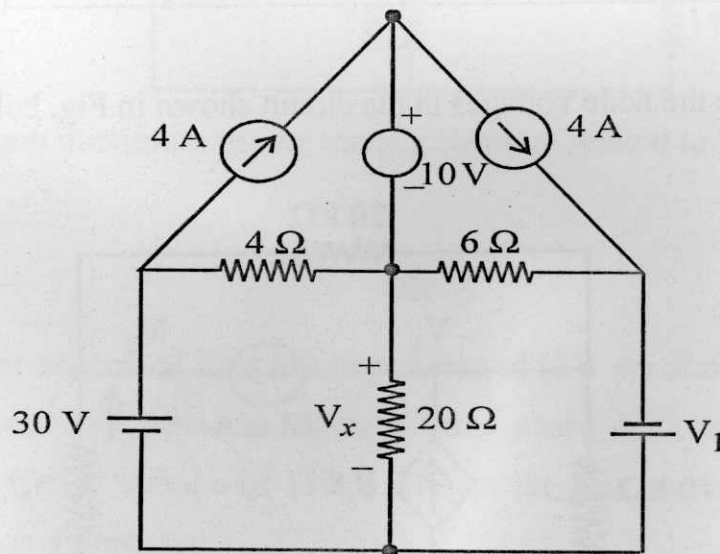1. (a) Using nodal analysis in the circuit shown in Fig. below, determine what value of V_1 cause V_x is equal to zero. (CO1, CO2)




P. T. O.


(2)

TEE-301(ECA)

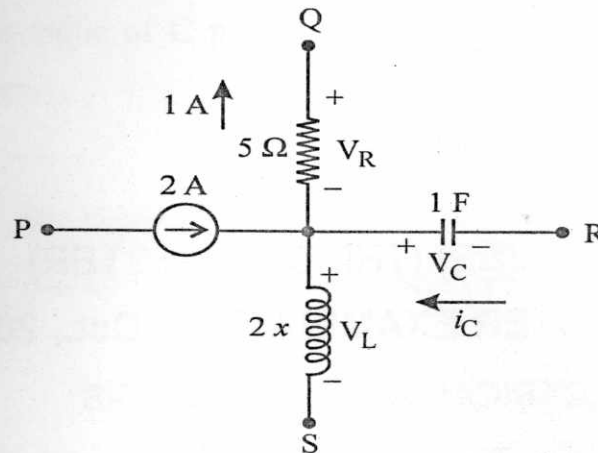
- (b) A segment of a circuit is shown in figure below. $V_R = 5 \text{ V}$, $V_C = 4 \sin 2t$. Find the voltage across the inductor. (CO1, CO2)



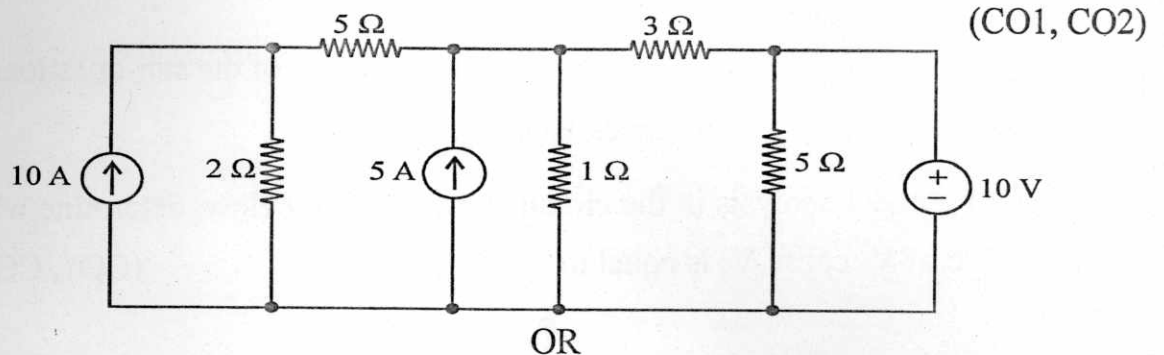2. (a) Find the current in the 3Ω resistor for the circuit shown in Fig. below :



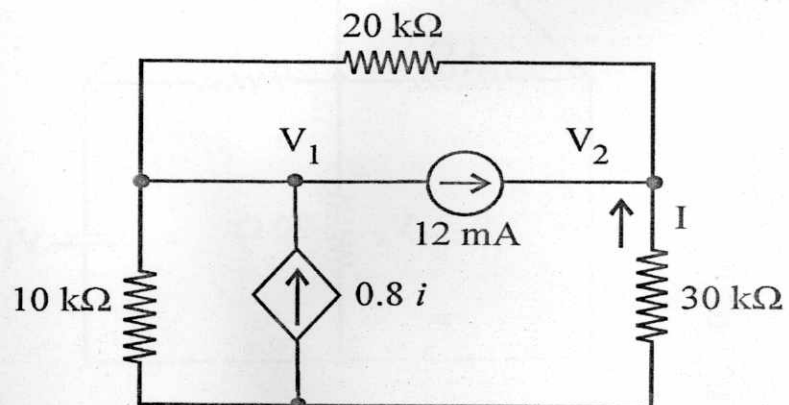
- (b) Calculate the node voltages in the circuit shown in Fig. below :



(3)


TEE-301(ECA)

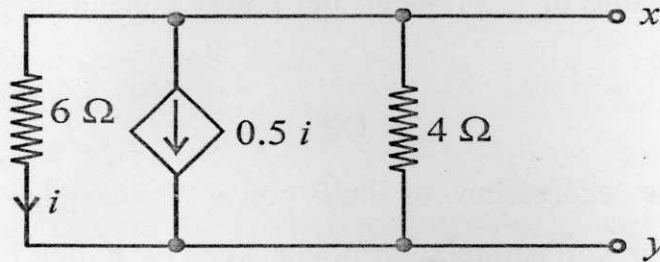3. (a) Find the Norton's equivalent circuit to the left of the terminal $x-y$ as shown in Fig. below : (CO1, CO2)



OR

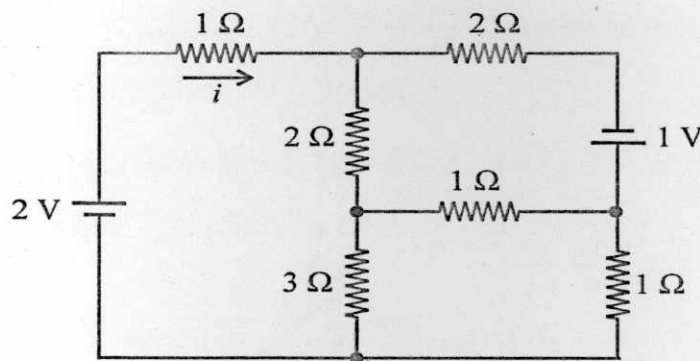- (b) Find the network shown in the figure, draw the oriented graph and obtain the tie set matrix. Use this matrix to find current i . (CO1, CO2)



4. (a) Explain maximum power transfer theorem related to AC circuits.

(CO1, CO3)

OR

- (b) A star connected load has impedance of $(3 + 4i)$ ohm in each phase and is connected across a balanced three phase delta connected alternator having line voltage of 120 V . Obtain the line current of both the load and generator. (CO1, CO3)

P. T. O.

5. (a) A series resonating circuit has a source frequency of 5 kHz and source impedance of $(2 + 4i)$ ohm. The load impedance being $(10 - iX_c)$ ohm. Find the value of C provided the power consumed by the resistor is maximum. (CO1, CO3)

OR

- (b) Derive the expression of half power frequencies in series RLC resonating circuit and relationship between F_0 , F_1 and F_2 . (CO1, CO3)