

Roll No.:

MID SEMESTER EXAMINATION SEPTEMBER 2025

Name of the Program: B. Tech

Semester: III

Name of the Course: Networks Analysis and Synthesis



Course Code: TEC 303



Time: 90 Minutes

Maximum Marks: 50

Note:

- i. Answer all the questions by choosing any one of the sub questions
- ii. Each questions carries 10 marks

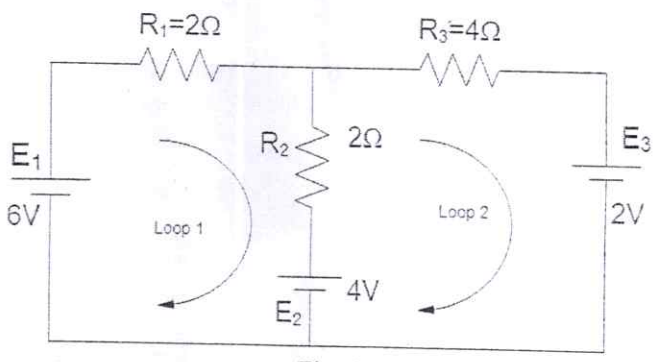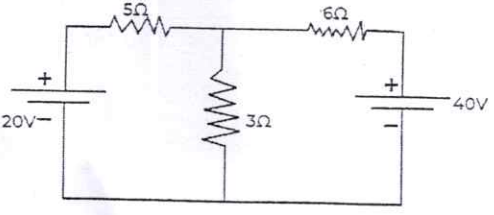Q1		10 Marks	CO1
(a)	Use mesh analysis find the loop currents of Fig. 1.		
	 Fig. 1		
	OR		
(b)	Find the power for the 6V source and indicate whether the source is delivering or absorbing power, from Fig. 1 above.		
Q2		10 Marks	CO1 CO2
(a)	A circuit consists of a battery of 18 V and three resistors: $R_1=3\ \Omega$, $R_2=6\ \Omega$, and $R_3=9\ \Omega$. Resistors R_1 and R_2 are connected in parallel, and their combination is connected in series with R_3 . Calculate the equivalent resistance of the circuit and current in each resistor (R_1 , R_2 , and R_3)		
	OR		
(b)	Find the current through 6 Ω resistor using superposition theorem in Fig. 2.		
	 Fig. 2		

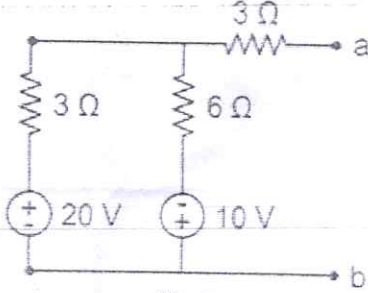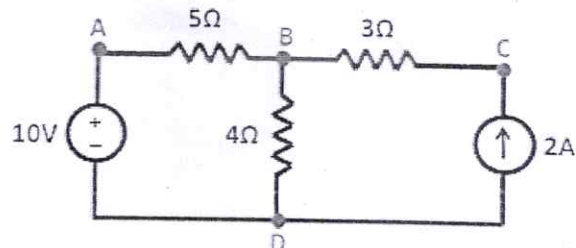Q3		10 Marks	CO1 CO2																																			
(a)	Find the Thevenin's equivalent circuit (V_{th} and R_{th}) across ab terminal in Fig.3.																																					
 Fig.3																																						
OR																																						
(b)	Define the following terms, (I) Link (II) Graph (III) Tree (IV) Node (V) Branch (VI) Twig of the following network and find incidence matrix.																																					
 Fig.4																																						
Q4		10 Marks	CO2																																			
(a)	Draw the oriented graph of the network with fundamental cut set matrix as shown																																					
<table border="1" style="margin-left: auto; margin-right: auto;"> <tr> <th>Branches =</th><th>1</th><th>2</th><th>3</th><th>4</th><th>5</th><th>6</th></tr> <tr> <td>Cutsets</td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr> <td>C_2</td><td>+1</td><td>+1</td><td>0</td><td>0</td><td>-1</td><td>0</td></tr> <tr> <td>C_3</td><td>0</td><td>0</td><td>-1</td><td>0</td><td>+1</td><td>-1</td></tr> <tr> <td>C_4</td><td>-1</td><td>0</td><td>0</td><td>-1</td><td>0</td><td>+1</td></tr> </table>				Branches =	1	2	3	4	5	6	Cutsets							C_2	+1	+1	0	0	-1	0	C_3	0	0	-1	0	+1	-1	C_4	-1	0	0	-1	0	+1
Branches =	1	2	3	4	5	6																																
Cutsets																																						
C_2	+1	+1	0	0	-1	0																																
C_3	0	0	-1	0	+1	-1																																
C_4	-1	0	0	-1	0	+1																																
OR																																						
(b)	Explain maximum power transfer theorem and reciprocity theorem with a proper example?																																					
Q5		10 Marks	CO1 CO3																																			
(a)	Explain Superposition Theorem and its limitations. Solve an example to illustrate its use.																																					
OR																																						
(b)	In the circuit shown below, the switch "s" is open at $t=0$, with zero initial conditions, find v , dv/dt , d^2v/dt^2 at $t=0^+$																																					

